

## Program Counter

### Main Code

See Appendix A

### Testbench

See Appendix B

### Simulation

 


Figure 1. Simulation of Program counter over 30 ns.

The Program Counter (PC) takes in a 16-bit input (PC\_in) and immediately sends that same value to a 16-bit output (PC\_out). Therefore, at 6ns when PC\_in = 1010\_1011\_1100\_1101, PC\_out outputs the same value. However, when reset is high, PC\_out will reset to 0000\_0000\_0000\_0000, no matter what value is input to the PC as shown in **Figure 1** at 18ns.

## Adders

### Main Code

See Appendix C

### Testbench

See Appendix D

### Simulation

 


Figure 2. Simulation of Adders over 30 ns.

The Adder module has two different functions which is written to two different 16-bit outputs (out1 & out2). One adder takes a 16-bit input (a), adds 1 to it, and writes it to output (out1); whereas the other adder takes two 16-bit inputs (a & b), adds them together, and writes it to output (out2). At the start of the simulation, the functionality of the adders was tested using signed negative numbers -5 (1111\_1111\_1111\_1101) and -3 (1111\_1111\_1111\_1011). The simulation gave the following output:

$$\begin{aligned}a &= -5 \\b &= -3 \\out1 &= a + 1'b1 = 1111111111111101 = fffe \\out2 &= a + b = 1111111111111101 + 1111111111111011 = fff8\end{aligned}$$

However, when reset is high both outputs are reset to 0000\_0000\_0000\_0000 as shown in **Figure 2** at 12ns.

## 2:1 MUX

### Main Code

See Appendix E

### Testbench

See Appendix F

### Simulation

 


Figure 3. Simulation of 2-to-1 MUX over 50ns.

The MUX module takes in two 16-bit inputs (a & b) and a 1-bit select line (sel). One of the inputs is then written to a 16-bit output (out) depending on the value of the select line. When the select line is 0, then the output is a; however, when the select line is 1, then the output is b. In **Figure 3** from 0-5ns when the select line is 0, then the output is 0000\_0000\_0000\_0001 (a); however, from 5-10ns when the select line is 1, then the output is 0000\_0000\_0000\_0010 (b).

# AND Gate

## Main Code

See Appendix G

## Testbench

See Appendix H

## Simulation

 


Figure 4. Simulation of AND gate over 25ns.

The AND gate module takes two 1-bit inputs (a & b), compares them using an AND gate, and writes the result to a 1-bit output (y). The simulation in Figure 4 shows the following results:

- 0 - 5ns, a = 0, b = 0, y = 0
- 5 - 10ns, a = 0, b = 1, y = 0
- 10 - 15ns, a = 1, b = 0, y = 0
- 15 - 20ns, a = 1, b = 1, y = 1

## Control Unit

### Main Code

See Appendix I

### Testbench

See Appendix J

### Simulation

 


Figure 5. Simulation of the Control Unit over 105ns.

The Control Unit takes in a 4-bit input (opcode) and assigns it to several control signal outputs (branch, mem2reg, mem\_read, mem\_write, alu\_src, alu\_op, & reg\_write). This portion of the project may vary based on the student's ISA. The control signals are shown below in **Table 1**. When observing the simulation in **Figure 5**, the opcode input 1110 (jmp instruction) matches the expected output values as shown in **Table 1**. The table can be used to verify the correct output of other input values in the simulation.

Table 1. Control Signals for Control Unit.

Instruction	Branch	Mem2Reg	MemRead	MemWrite	ALU Source	ALU Opcode	RegWrite
plus	0	0	0	0	0	00	1
min	0	0	0	0	0	01	1
and	0	0	0	0	0	10	1
or	0	0	0	0	0	11	1
ldw	0	1	1	0	1	00	1
stw	0	1	0	1	1	00	0
plusi	0	0	0	0	1	00	1
lui	0	0	0	0	0	xx	0
beq	1	x	0	0	0	01	0
bne	1	x	0	0	0	01	0
bgt	1	x	0	0	0	01	0
blt	1	x	0	0	0	01	0
bge	1	x	0	0	0	01	0
blte	1	x	0	0	0	01	0
jmp	1	1	0	0	x	xx	0
stop	0	0	0	0	0	xx	0

## Register File

### Main Code

See Appendix K

### Testbench

See Appendix L

### Simulation

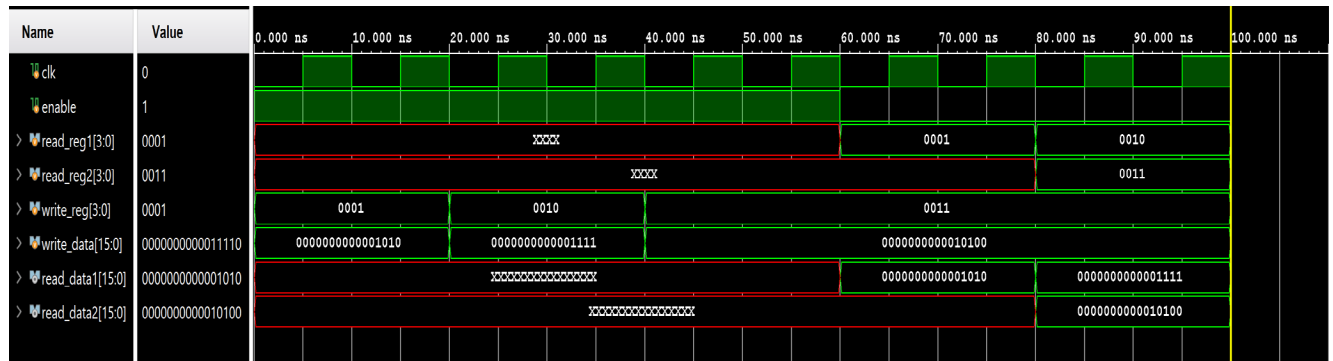


Figure 6. Simulation of Register File over 100ns.

The Register File module has three 4-bit inputs (read\_reg1, read\_reg2, & write\_reg), one 16-bit input (write\_data), and an enable. The 1-bit enable line is used to signal a data write operation on the Register File. The enable line is active high. When there are valid register numbers in the output selection ports read\_reg1 and read\_reg2 then the Register File outputs the values in the corresponding registers to the output ports read\_data1 and read\_data2. When the enable line is high and there is a valid register number in the input selection port write\_reg then the Register File writes the value on the input port write\_data to the corresponding register in the Register File as shown in **Figure 6**.

# ALU

## Main Code

See Appendix M

## Testbench

See Appendix N

## Simulation

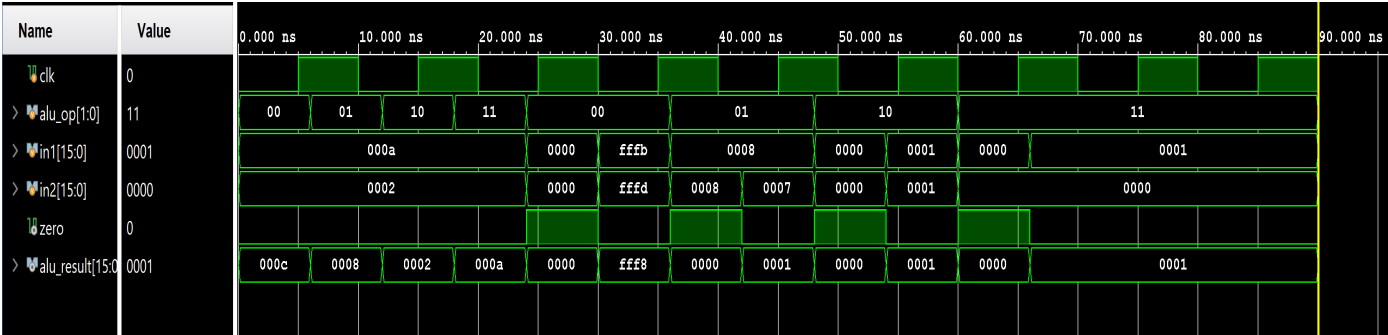


Figure 7. Simulation of ALU over 90ns.

The ALU takes in two 16-bit values (*in1* & *in2*) and a 2-bit input (*alu\_op*). The input *alu\_op* performs one of the following four functions on inputs *in1* & *in2*: ADD, SUB, AND, OR. The result is then output to a 16-bit output (*alu\_result*) and a 1-bit output (*zero*). The output *zero* only goes high when *alu\_result* equals 0. The following test was performed on the simulation to test functionality at 25ns as shown in **Figure 7**:

$$\begin{aligned} in1 &= 0000 \\ in2 &= 0000 \\ alu_{op} &= 00 = ADD \\ alu_{result} &= in1 + in2 = 0000 \\ 0 &= 0, so zero = 1 \end{aligned}$$

The following test was performed on the simulation to test functionality at 30ns as shown in **Figure 7**:

$$\begin{aligned} in1 &= -3 = fffb \\ in2 &= -5 = fffd \\ alu_{op} &= 00 = ADD \\ alu_{result} &= in1 + in2 = -8 = fffe \\ -8 &\neq 0, so zero = 0 \end{aligned}$$

## Immediate Generator

### Main Code

See Appendix O

### Testbench

See Appendix P

### Simulation

 


Figure 8. Simulation of Immediate Generator over 25ns.

The Immediate Generator takes in one 4-bit input (`imm_in`) and extends the MSB of that input by 12-bits to produce a 16-bit output (`out`). As seen in **Figure 8**, the following outputs are produced in the simulation:

- `Imm_in = 0000`, `out = 0000000000000000`
- `Imm_in = 0111`, `out = 0000000000000111`
- `Imm_in = 1111`, `out = 1111111111111111`
- `Imm_in = 1110`, `out = 1111111111111110`

The MSB is highlighted in green, and the copied bits are highlighted in red.



## Appendix A

```
module PC(  
    input rst,clk,  
    input [15:0] PC_in,  
    output reg [15:0] PC_out  
);  
initial  
    begin  
        PC_out <= 16'h0000;  
    end  
always @ (*)  
    begin  
        if(rst) PC_out <= 16'h0000;  
        else PC_out = PC_in;  
    end  
endmodule
```

## Appendix B

```
module PC_tb;
    reg rst, clk;
    reg [15:0] PC_in;
    wire [15:0] PC_out;

    PC uut(.rst(rst),.PC_in(PC_in),.PC_out(PC_out));
    initial
        begin
            clk = 0;
            rst = 0;
            forever
                #5 clk = ~clk;
        end
    initial
        begin
            PC_in = 16'h0;
            #6;
            PC_in = 16'habcd;
            #6;
            PC_in = 16'hefab;
            #6;
            PC_in = 16'habcd;
            rst = 1;
            #6;
            PC_in = 16'hffff;
            rst = 0;
            #6;
        end
endmodule
```

## Appendix C

```
module Adders(  
    input rst, clk,  
    input [15:0] a, b,  
    output reg [15:0] out1, out2  
);  
always @ (clk or rst)  
    begin  
        if(rst) begin  
            out1 <= 16'h0000;  
            out2 <= 16'h0000;  
        end  
        else if (clk)  
            begin  
                out1 <= a + 1'b1;  
                out2 <= a + b;  
            end  
    end  
end  
endmodule
```

## Appendix D

```
module Adders_tb;
    reg clk,rst;
    reg [15:0] a, b;
    wire [15:0] out1,out2;

    Adders uut(.clk(clk),.rst(rst),
               .a(a),.b(b),
               .out1(out1),.out2(out2));
    initial
        begin
            clk = 0;
            rst = 0;
            forever
                #5 clk = ~clk;
        end
    initial
        begin
            a = 16'h1;
            b = 16'h000f;
            #6;
            a = 16'h2;
            b = 16'h000a;
            #6;
            a = 16'hab00;
            b = 16'h000b;
            rst = 1;
            #6
            a = 16'h3;
            b = 16'h000b;
            rst = 0;
            #6;
        end
endmodule
```

## Appendix E

```
module Mux(  
    input [15:0] a,b,  
    input wire sel,  
    output reg [15:0] out  
);  
always @ (a or b or sel)  
begin  
    case (sel)  
        1'b0: out <= a;  
        1'b1: out <= b;  
    endcase  
end  
endmodule
```

## Appendix F

```
module Mux_tb;
    reg sel;
    reg [15:0] a,b;
    wire [15:0] out;
    reg count = 1'b1;

    Mux uut(.a(a),.b(b),.sel(sel),.out(out));
    initial
        begin
            a = 16'h0; b = 16'h0; sel = 1'b0;
            for(count = 1'b0;count<256;count = count+1'b1) begin
                a = a + 16'h01;
                b = b + 16'h02;
                #10;
            end
        end
    always #5 sel = ~sel;
endmodule
```

## Appendix G

```
module AND_gate(  
    input a, b,  
    output reg y  
);  
always @ (a or b)  
begin  
    if(a == 1'b1 && b == 1'b1) begin  
        y = 1'b1;  
    end  
    else  
        y = 1'b0;  
    end  
endmodule
```

## Appendix H

```
module AND_gate_tb;
    reg a, b;
    wire y;

    AND_gate AND1(.a(a),.b(b),.y(y));

    initial
        begin
            a = 0; b = 0;
            a = 0; b = 0; #5;
            a = 0; b = 1; #5;
            a = 1; b = 0; #5;
            a = 1; b = 1; #5;
        end
endmodule
```



## Appendix I

```
module Control_Unit(
    input [3:0] opcode,
    output reg [1:0] alu_op,
    output reg branch, mem2reg, mem_read, mem_write,
           alu_src, reg_write
);
always @ (*)
begin
    case(opcode)
        4'b0000:    //plus
        begin
            branch = 1'b0;
            mem2reg = 1'b0;
            mem_read = 1'b0;
            mem_write = 1'b0;
            alu_src = 1'b0;
            alu_op = 2'b00;
            reg_write = 1'b1;
        end
        4'b0001:    //min
        begin
            branch = 1'b0;
            mem2reg = 1'b0;
            mem_read = 1'b0;
            mem_write = 1'b0;
            alu_src = 1'b0;
            alu_op = 2'b01;
            reg_write = 1'b1;
        end
        4'b0010:    //and
        begin
            branch = 1'b0;
            mem2reg = 1'b0;
            mem_read = 1'b0;
            mem_write = 1'b0;
            alu_src = 1'b0;
            alu_op = 2'b10;
            reg_write = 1'b1;
        end
        4'b0011:    //or
        begin
            branch = 1'b0;
            mem2reg = 1'b0;
            mem_read = 1'b0;
            mem_write = 1'b0;
            alu_src = 1'b0;
            alu_op = 2'b11;
            reg_write = 1'b1;
        end
        4'b0100:    //ldw
        begin
            branch = 1'b0;
            mem2reg = 1'b1;
            mem_read = 1'b1;
            mem_write = 1'b0;
        end
    endcase
end
```

```

        alu_src = 1'b1;
        alu_op = 2'b00;
        reg_write = 1'b1;
    end
4'b0101:    //stw
    begin
        branch = 1'b0;
        mem2reg = 1'b1;
        mem_read = 1'b0;
        mem_write = 1'b1;
        alu_src = 1'b1;
        alu_op = 2'b00;
        reg_write = 1'b0;
    end
4'b0110:    //plusi
    begin
        branch = 1'b0;
        mem2reg = 1'b0;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'b1;
        alu_op = 2'b00;
        reg_write = 1'b1;
    end
4'b0111:    //lui
    begin
        branch = 1'b0;
        mem2reg = 1'b0;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'b0;
        alu_op = 2'bxx;
        reg_write = 1'b0;
    end
4'b1000:    //beq
    begin
        branch = 1'b1;
        mem2reg = 1'bx;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'b0;
        alu_op = 2'b01;
        reg_write = 1'b0;
    end
4'b1001:    //bne
    begin
        branch = 1'b1;
        mem2reg = 1'bx;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'b0;
        alu_op = 2'b01;
        reg_write = 1'b0;
    end
4'b1010:    //bgt
    begin
        branch = 1'b1;

```

```

        mem2reg = 1'bx;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'b0;
        alu_op = 2'b01;
        reg_write = 1'b0;
    end
4'b1011:    //blt
    begin
        branch = 1'b1;
        mem2reg = 1'bx;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'b0;
        alu_op = 2'b01;
        reg_write = 1'b0;
    end
4'b1100:    //bge
    begin
        branch = 1'b1;
        mem2reg = 1'bx;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'b0;
        alu_op = 2'b01;
        reg_write = 1'b0;
    end
4'b1101:    //blte
    begin
        branch = 1'b1;
        mem2reg = 1'bx;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'b0;
        alu_op = 2'b01;
        reg_write = 1'b0;
    end
4'b1110:    //jmp
    begin
        branch = 1'b1;
        mem2reg = 1'b1;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'bx;
        alu_op = 2'bxx;
        reg_write = 1'b0;
    end
4'b1111:    //stop
    begin
        branch = 1'b0;
        mem2reg = 1'b0;
        mem_read = 1'b0;
        mem_write = 1'b0;
        alu_src = 1'b0;
        alu_op = 2'bxx;
        reg_write = 1'b0;
    end
end

```

## Appendix J

```
module Control_Unit_tb;
    reg clk;
    reg [3:0] opcode;
    wire [1:0] alu_op;
    wire branch, mem2reg, mem_read, mem_write,
        alu_src, reg_write;

    Control_Unit uut(.opcode(opcode), .alu_op(alu_op),
                    .branch(branch), .mem2reg(mem2reg),
                    .mem_read(mem_read), .mem_write(mem_write),
                    .alu_src(alu_src), .reg_write(reg_write));

    initial
        begin
            clk = 0;
            forever
                #5 clk = ~clk;
        end
    initial
        begin
            #6 opcode = 4'b0000;
            #6 opcode = 4'b0001;
            #6 opcode = 4'b0010;
            #6 opcode = 4'b0011;
            #6 opcode = 4'b0100;
            #6 opcode = 4'b0101;
            #6 opcode = 4'b0110;
            #6 opcode = 4'b0111;
            #6 opcode = 4'b1000;
            #6 opcode = 4'b1001;
            #6 opcode = 4'b1010;
            #6 opcode = 4'b1011;
            #6 opcode = 4'b1100;
            #6 opcode = 4'b1101;
            #6 opcode = 4'b1110;
            #6 opcode = 4'b1111;
        end
endmodule
```

## Appendix K

```
module RegFile(
    input enable,clk,
    input [3:0] read_reg1,read_reg2,write_reg,
    input [15:0] write_data,
    output reg [15:0] read_data1,read_data2
);
    reg [15:0] registers [0:15];    //16 16-bit registers
    integer i;
initial
    begin
        for(i=0;i<16;i=i+1)
            registers[i] <= 16'd0;
    end
always @ (posedge clk)
    begin
        if(enable) begin
            registers[write_reg] <= write_data;
        end
        //output selected registers
        assign read_data1 = registers[read_reg1];
        assign read_data2 = registers[read_reg2];
    end
endmodule
```

## Appendix L

```
module regfile_tb;
//inputs
reg clk,enable;//rst;
reg [3:0] read_reg1,read_reg2,write_reg;
reg [15:0] write_data;
//outputs
wire [15:0] read_data1,read_data2;

RegFile UUT(.clk(clk),
            .enable(enable),
            .read_reg1(read_reg1),
            .read_reg2(read_reg2),
            .write_reg(write_reg),
            .write_data(write_data),
            .read_data1(read_data1),
            .read_data2(read_data2));

initial
begin
    clk = 0;
    enable = 0;
    //rst = 0;
    forever
        #5 clk = ~clk;
    end
initial
begin
    write_reg = 1;
    enable = 1;
    write_data = 10;
    #20;
    write_reg = 2;
    enable = 1;
    write_data = 15;
    #20;
    write_reg = 3;
    enable = 1;
    write_data = 20;
    #20;
    read_reg1 = 1;
    enable = 0;
    #20;
    read_reg1 = 2;
    read_reg2 = 3;
    #20;
    read_reg1 = 1;
    write_reg = 1;
    enable = 1;
    write_data = 30;
    #20;
end
endmodule
```

## Appendix M

```
module ALU(
    input [15:0] in1,in2,
    input [1:0] alu_op,
    output reg [15:0] alu_result,
    output reg zero
);
    wire [16:0] temp;

    //ALU Opcodes
    localparam ADD = 2'b00;
    localparam SUB = 2'b01;
    localparam AND = 2'b10;
    localparam OR = 2'b11;
always @ (*)
    begin
        case(alu_op)
            ADD: alu_result = in1 + in2;    //ADD
            SUB: alu_result = in1 - in2;    //SUB
            AND: alu_result = in1 & in2;    //AND
            OR: alu_result = in1 | in2;    //OR
            default: alu_result = in1 + in2; //default
        endcase
        if(alu_result == 0)
            zero = 1'b1;
        else
            zero = 1'b0;
        end
    end
endmodule
```

## Appendix N

```
module ALU_tb;
    reg clk;
    reg [1:0] alu_op;
    reg [15:0] in1,in2;
    wire zero;
    wire [15:0] alu_result;
    integer i = 2'd0;
    ALU uut(.in1(in1),.in2(in2),
        .alu_op(alu_op),.alu_result(alu_result),
        .zero(zero));
    initial
        begin
            clk = 0;
            forever
                #5 clk = ~clk;
        end
    initial
        begin
            in1 = 16'h000a; in2 = 16'h0002; alu_op = 2'b0;
            for(i=0;i<=3;i=i+1'b1) begin
                alu_op = i;
                #6;
            end
            //Test ADD: first add sets zero flag high and second add resets zero flag
            in1 = 16'h0;
            in2 = 16'h0;
            alu_op = 2'b00;
            #6;
            in1 = 16'hffffb;
            in2 = 16'hffffd;
            alu_op = 2'b00;
            #6;
            //Test SUB: first sub sets zero flag high and second sub resets zero flag
            in1 = 16'h8;
            in2 = 16'h8;
            alu_op = 2'b01;
            #6;
            in1 = 16'h8;
            in2 = 16'h7;
            alu_op = 2'b01;
            #6;
            //Test AND: first AND sets zero flag high and second AND resets zero flag
            in1 = 16'h0;
            in2 = 16'h0;
            alu_op = 2'b10;
            #6;
            in1 = 16'h1;
            in2 = 16'h1;
            alu_op = 2'b10;
            #6;
            //Test OR: first OR sets zero flag high and second OR resets zero flag
            in1 = 16'h0;
            in2 = 16'h0;
            alu_op = 2'b11;
            #6;
```



```
        in1 = 16'h1;  
        in2 = 16'h0;  
        alu_op = 2'b11;  
        #6;  
    end  
endmodule
```

## Appendix O

```
module ImmGen(  
    input clk,  
    input [3:0] imm_in,  
    output reg [15:0] out  
);  
    wire [3:0] imm;  
    assign imm = imm_in;  
    //sign extension of input assigned to output  
always @ (*)  
    begin  
        out [15:0] <= {{12{imm[3]}}, imm[3:0]};  
    end  
endmodule
```

## Appendix P

```
module ImmGen_tb;
//inputs
reg clk;
reg [3:0] imm_in;
//outputs
wire [15:0] out;

ImmGen UUT(.clk(clk),.imm_in(imm_in),.out(out));
    initial
        begin
            clk = 0;
            forever
                #5 clk = ~clk;
        end
    initial
        begin
            imm_in = 4'd0;
        end
    initial
        begin
            #6 imm_in = 4'b0111;
            #12 imm_in = 4'b1111;
            #3  imm_in = 4'b1110;
        end
endmodule
```